

1. Write the following sinusoids as phasors

$$V_1(t) = 156 \cos(110\pi t + 60^\circ)$$

$$V_2(t) = 220 \cos(120\pi t - 45^\circ)$$


2. Write the following phasors as sinusoids. $\omega = 20 \text{ rad/sec}$

$$\bar{V}_1 = 20 \angle 15^\circ$$


$$\bar{V}_2 = 10 \angle 45^\circ$$

$$\bar{V}_3 = \bar{V}_1 + \bar{V}_2$$

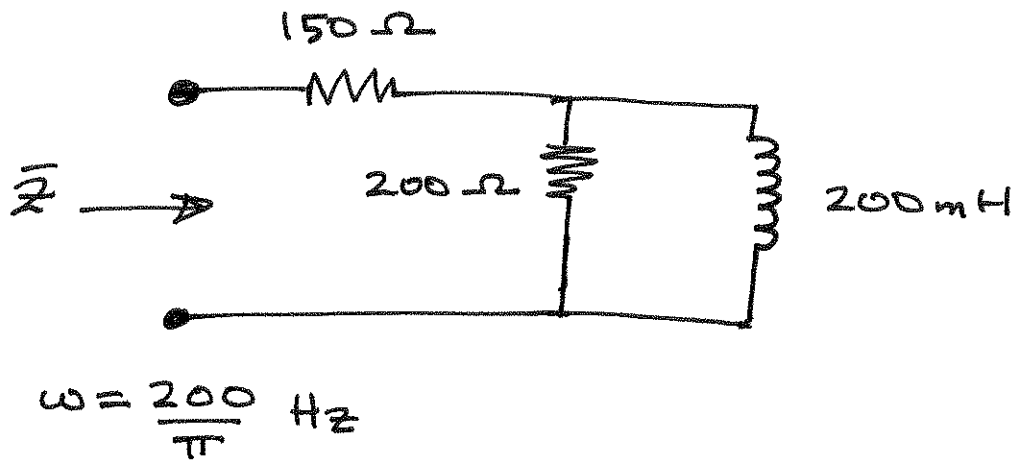3. Find the total impedance of the circuit.



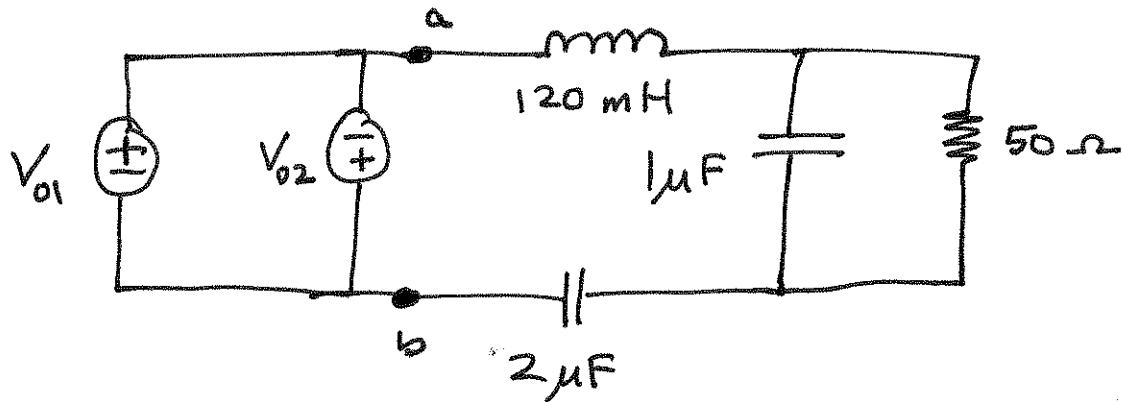
4. What is \bar{Z}_{eq} as seen by the two voltage sources? (or to the right of nodes a and b)



$$\omega = 250 \frac{\text{rad}}{\text{sec}}$$


$$V_{01} = 20 \angle 18^\circ \quad V_{02} = 18 \angle 20^\circ$$

5.

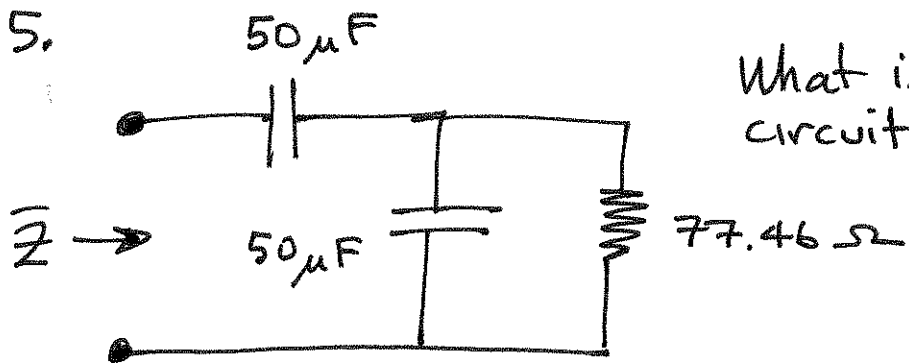


What is ω for the circuit if $\bar{Z} = 40.4125 - j137.5\Omega$

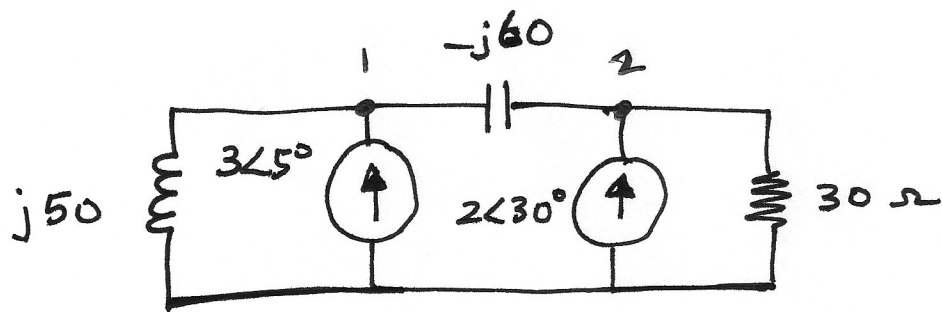6. Find voltages \bar{V}_1 and \bar{V}_2 .




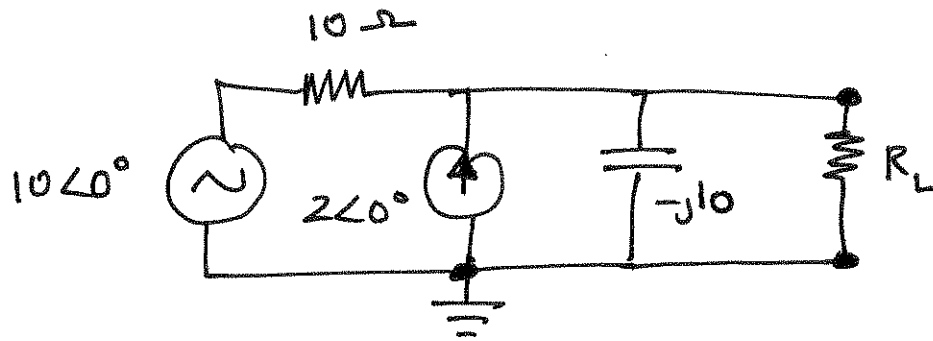7. Find the Thevenin equivalent circuit as seen by the load resistor.




8. Find the Norton equivalent circuit for the circuit in problem 7.

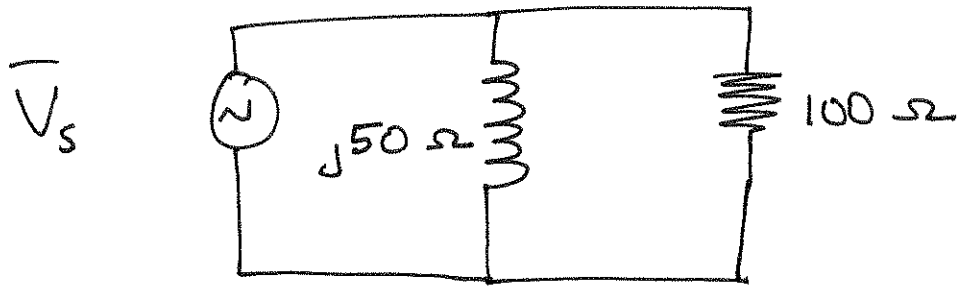9. Find the average power & reactive power generated by the resistor in the circuit if $\bar{V}_S = 160 \angle 30^\circ$



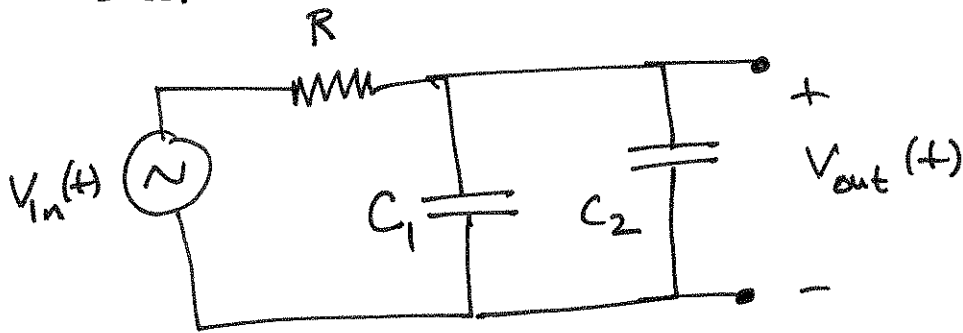10. Find the transfer function. Write the magnitude in terms of decibels.



$$R = \frac{500}{\pi} \, \Omega$$

$$C_1 = 3.75 \, \mu\text{F}$$

$$C_2 = 7.5 \, \mu\text{F}$$